```
% Patrobas Adewumi
% 100963608
% ELEC 4700
% assignment4
clear all
runTime = 1; % in seconds
timecuts = 1000;
dt = runTime/timecuts;
Cn = 0.00001;
R1 = 1;
C1 = 0.25;
R2 = 2i
L1 = 0.2;
R3 = 10;
a = 100;
R4 = 0.1;
Ro = 1000;
C = [0, 0,
              0, 0, 0, 0, 0, 0; ... V1
    -C1,C1,
            0, 0, 0, 0, 0, 0; ... V2
      0, 0, -L1, 0, 0, 0, 0, 0; ... I1
      0,0,
              0, Cn, 0, 0, 0; ... V3
      0,0,
              0, 0, 0, 0, 0; ... I3
              0, Cn, 0, 0, 0; ... V4
      0,0,
      0,0,
              0, 0, 0, 0, 0; ... In
      0,0,
              0, 0, 0, 0, 0]; %Vo
   응
        V1
                       V2 I1
                                V3 I3
                                           V4 In
                                                            Vo
G = [
                       0, 0,
                                0, 0,
        1,
                                           0, 0,
                                                             0; ...
V1
     -1/R1, (1/R2 + 1/R1), -1,
                                0, 0,
                                            0, 0,
                                                             0; ...
V2
         0,
                        1, 0,
                                -1, 0,
                                            0, 0,
                                                             0; ...
I1
                       0, -1, 1/R3, 0,
                                            0, -1,
                                                             0; ...
         0,
V3
                       0, 0, 0, -a,
         0,
                                            1, 0,
                                                             0; ...
I3
                       0, 0, 1/R3, -1,
                                            0, -1,
                                                             0; ...
         0,
V4
                        0, 0,
                                 0, 0,
                                            0, 1,
                                                             0; ...
         0,
 Tn
                        0, 0,
                                0, 0, -1/R4, 0, (1/R4 + 1/R0)];
         0,
 %Vo
disp('Question 3: G and C matrices:')
disp(G)
disp(C)
```

1

```
% Gaussian Pulse Function
mag = 1;
dev = 0.03;
delay = 0.06;
Flist = zeros(8,1,timecuts);
for count = 1:1:timecuts
   Flist(1,1,count) = mag*exp(-((count*dt-delay)/dev)^2);
   Flist(7,1,count) = 0.001*randn;
end
Vlist = zeros(8,1,timecuts);
for count = 2:1:timecuts
   A = C/dt +G;
   Vlist(:,:,count) = A\(C*Vlist(:,:,count-1)/dt +Flist(:,:,count));
end
V1list(1,:) = Vlist(1,1,:);
V2list(1,:) = Vlist(2,1,:);
ILlist(1,:) = Vlist(3,1,:);
I3list(1,:) = Vlist(4,1,:);
V4list(1,:) = Vlist(5,1,:);
Inlist(1,:) = Vlist(7,1,:);
Volist(1,:) = Vlist(8,1,:);
figure(7)
plot((1:timecuts).*dt,Volist(1,:))
xlabel('Time(secs)')
ylabel('Voltage')
title('Vout of Gaussian Pulse with In and Cn')
plot((1:timecuts).*dt,V1list(1,:))
hold off
figure(8)
g = abs(fftshift(fft(Volist(1,:))));
plot(((1:length(g))/timecuts)-0.5,g)
xlim([-0.005 0.005])
xlabel('Frequency')
ylabel('Magnitude')
title('Fourier Transform of Output')
% Cn 1
Cn = 0.0001;
C = [0, 0, 0, 0, 0, 0, 0, 0; ... V1]
    -C1,C1,
             0, 0, 0, 0, 0; ... V2
      0, 0, -L1, 0, 0, 0, 0, 0; ... I1
      0,0,
            0, Cn, 0, 0, 0, 0; ... V3
      0,0,
            0, 0, 0, 0, 0, 0; ... I3
      0,0,
             0, Cn, 0, 0, 0, 0; ... V4
```

```
0, 0, 0, 0, 0, 0, 0; ... In
      0,0,
             0, 0, 0, 0, 0, 0]; %Vo
% Gaussian Pulse Function
mag = 1;
dev = 0.03;
delay = 0.06;
Flist = zeros(8,1,timecuts);
for count = 1:1:timecuts
   Flist(1,1,count) = mag*exp(-((count*dt-delay)/dev)^2);
   Flist(7,1,count) = 0.001*randn;
end
Vlist = zeros(8,1,timecuts);
for count = 2:1:timecuts
   A = C/dt +G;
   Vlist(:,:,count) = A\(C*Vlist(:,:,count-1)/dt +Flist(:,:,count));
end
V1list(1,:) = Vlist(1,1,:);
V2list(1,:) = Vlist(2,1,:);
ILlist(1,:) = Vlist(3,1,:);
I3list(1,:) = Vlist(4,1,:);
V4list(1,:) = Vlist(5,1,:);
Inlist(1,:) = Vlist(7,1,:);
Volist(1,:) = Vlist(8,1,:);
figure(9)
plot((1:timecuts).*dt,Volist(1,:))
xlabel('Time(secs)')
ylabel('Voltage')
title('Vout of Gaussian Pulse with In and Cn Cn=0.0001')
hold on
plot((1:timecuts).*dt,V1list(1,:))
hold off
figure(10)
g = abs(fftshift(fft(Volist(1,:))));
plot(((1:length(g))/timecuts)-0.5,g)
xlim([-0.05 0.05])
xlabel('Frequency')
ylabel('Magnitude')
title('Fourier Transform of Output')
% Cn 2
Cn = 0.001;
C = [0, 0, 0, 0, 0, 0, 0, 0; ... V1]
           0, 0, 0, 0, 0, 0; ... V2
    -C1,C1,
      0, 0, -L1, 0, 0, 0, 0, 0; ... I1
```

```
0, Cn, 0, 0, 0; ... V4
      0,0,
      0,0,
            0, 0, 0, 0, 0, 0; ... In
      0,0,
             0, 0, 0, 0, 0, 0]; %Vo
% Gaussian Pulse Function
mag = 1;
dev = 0.03;
delay = 0.06;
Flist = zeros(8,1,timecuts);
for count = 1:1:timecuts
   Flist(1,1,count) = mag*exp(-((count*dt-delay)/dev)^2);
   Flist(7,1,count) = 0.001*randn;
end
Vlist = zeros(8,1,timecuts);
for count = 2:1:timecuts
   A = C/dt +G;
   Vlist(:,:,count) = A(C*Vlist(:,:,count-1)/dt +Flist(:,:,count));
end
V1list(1,:) = Vlist(1,1,:);
V2list(1,:) = Vlist(2,1,:);
ILlist(1,:) = Vlist(3,1,:);
I3list(1,:) = Vlist(4,1,:);
V4list(1,:) = Vlist(5,1,:);
Inlist(1,:) = Vlist(7,1,:);
Volist(1,:) = Vlist(8,1,:);
figure(11)
plot((1:timecuts).*dt,Volist(1,:))
xlabel('Time(secs)')
ylabel('Voltage')
title('Vout of Gaussian Pulse with In and Cn Cn=0.001')
hold on
plot((1:timecuts).*dt,V1list(1,:))
hold off
figure(12)
g = abs(fftshift(fft(Volist(1,:))));
plot(((1:length(q))/timecuts)-0.5,q)
xlim([-0.05 0.05])
xlabel('Frequency')
ylabel('Magnitude')
title('Fourier Transform of Output')
% Cn 3
Cn = 0.01;
```

0, Cn, 0, 0, 0; ... V3

0, 0, 0, 0, 0, 0; ... I3

0, 0, 0, 0,

```
C = [0, 0, 0, 0, 0, 0, 0, 0; ... V1]
    -C1,C1,
            0, 0, 0, 0, 0, 0; ... V2
      0, 0, -L1, 0, 0, 0, 0, 0; ... I1
             0, Cn, 0, 0, 0; ... V3
      0,0,
            0, 0, 0, 0, 0, 0; ... I3
            0, Cn, 0, 0, 0; ... V4
      0,0,
             0, 0, 0, 0, 0; ... In
      0,0,
             0, 0, 0, 0, 0, 0]; %Vo
      0,0,
% Gaussian Pulse Function
mag = 1;
dev = 0.03;
delay = 0.06;
Flist = zeros(8,1,timecuts);
for count = 1:1:timecuts
   Flist(1,1,count) = mag*exp(-((count*dt-delay)/dev)^2);
   Flist(7,1,count) = 0.001*randn;
end
Vlist = zeros(8,1,timecuts);
for count = 2:1:timecuts
   A = C/dt +Gi
   Vlist(:,:,count) = A(C*Vlist(:,:,count-1)/dt +Flist(:,:,count));
end
V1list(1,:) = Vlist(1,1,:);
V2list(1,:) = Vlist(2,1,:);
ILlist(1,:) = Vlist(3,1,:);
I3list(1,:) = Vlist(4,1,:);
V4list(1,:) = Vlist(5,1,:);
Inlist(1,:) = Vlist(7,1,:);
Volist(1,:) = Vlist(8,1,:);
figure(13)
plot((1:timecuts).*dt,Volist(1,:))
xlabel('Time(secs)')
ylabel('Voltage')
title('Vout of Gaussian Pulse with In and Cn Cn=0.01')
hold on
plot((1:timecuts).*dt,V1list(1,:))
hold off
figure(14)
q = abs(fftshift(fft(Volist(1,:))));
plot(((1:length(g))/timecuts)-0.5,g)
xlim([-0.05 0.05])
xlabel('Frequency')
ylabel('Magnitude')
title('Fourier Transform of Output')
```

```
clear all
% changing timesteps
runTime = 1; % in seconds
timecuts = 100;
dt = runTime/timecuts;
Cn = 0.00001;
R1 = 1;
C1 = 0.25;
R2 = 2i
L1 = 0.2;
R3 = 10;
a = 100;
R4 = 0.1;
Ro = 1000;
C = [0, 0, 0, 0, 0, 0, 0, 0; ... V1]
    -C1,C1,
           0, 0, 0, 0, 0, 0; ... V2
      0, 0, -L1, 0, 0, 0, 0, 0; ... I1
            0, Cn, 0, 0, 0; ... V3
      0,0,
            0, 0, 0, 0, 0, 0; ... I3
      0,0,
      0,0,
            0, Cn, 0, 0, 0, 0; ... V4
     0,0,
            0, 0, 0, 0, 0, 0; ... In
      0,0,
            0, 0, 0, 0, 0, 0]; %Vo
  용
      V1
                    V2 I1
                           V3 I3
                                     V4 In
                                                    Vo
G = [
       1,
                     0, 0,
                            0, 0,
                                      0, 0,
                                                      0; ...
\nabla 1
     -1/R1, (1/R2 + 1/R1), -1, 0, 0,
                                      0, 0,
                                                      0; ...
V2
                                                      0; ...
        0,
                     1, 0, -1, 0,
                                      0, 0,
I1
                    0, -1, 1/R3, 0,
                                      0, -1,
        0,
                                                      0; ...
V3
                    0, 0, 0, -a,
        0,
                                       1, 0,
                                                      0; ...
I3
        0,
                    0, 0, 1/R3, -1,
                                       0, -1,
                                                      0; ...
V4
                    0, 0,
                            0, 0,
                                       0, 1,
        0,
                                                      0; ...
In
                    0, 0,
                            0, 0, -1/R4, 0, (1/R4 + 1/R0)];
        0,
 %Vo
% Gaussian Pulse Function
mag = 1;
dev = 0.03;
delay = 0.06;
Flist = zeros(8,1,timecuts);
for count = 1:1:timecuts
   Flist(1,1,count) = mag*exp(-((count*dt-delay)/dev)^2);
   Flist(7,1,count) = 0.001*randn;
```


```
end
Vlist = zeros(8,1,timecuts);
for count = 2:1:timecuts
    A = C/dt +G;
    Vlist(:,:,count) = A(C*Vlist(:,:,count-1)/dt +Flist(:,:,count));
end
V1list(1,:) = Vlist(1,1,:);
V2list(1,:) = Vlist(2,1,:);
ILlist(1,:) = Vlist(3,1,:);
I3list(1,:) = Vlist(4,1,:);
V4list(1,:) = Vlist(5,1,:);
Inlist(1,:) = Vlist(7,1,:);
Volist(1,:) = Vlist(8,1,:);
figure(15)
plot((1:timecuts).*dt,Volist(1,:))
xlabel('Time(secs)')
ylabel('Voltage')
title('Vout of Gaussian Pulse with In and Cn timesteps=100')
plot((1:timecuts).*dt,V1list(1,:))
hold off
figure(16)
g = abs(fftshift(fft(Volist(1,:))));
plot(((1:length(g))/timecuts)-0.5,g)
xlim([-0.5 0.5])
xlabel('Frequency')
ylabel('Magnitude')
title('Fourier Transform of Output')
% Timestep
clear all
runTime = 1;
timecuts = 10000;
dt = runTime/timecuts;
R1 = 1;
C1 = 0.25;
R2 = 2;
L1 = 0.2;
R3 = 10;
a = 100;
R4 = 0.1;
Ro = 1000;
Cn = 0.00001;
C = [0, 0, 0, 0, 0, 0, 0, 0; ... V1]
             0, 0, 0, 0, 0, 0; ... V2
     -C1,C1,
       0, 0, -L1, 0, 0, 0, 0, 0; ... I1
```


```
0, Cn, 0, 0, 0; ... V3
      0,0,
      0,0,
             0, 0, 0, 0, 0, 0; ... I3
      0,0,
            0, Cn, 0, 0, 0; ... V4
            0, 0, 0, 0, 0; ... In
      0,0,
      0,0,
            0, 0, 0, 0, 0, 0]; %Vo
                    V2 I1 V3 I3
  응
       V1
                                      V4 In
                                                     Vo
G = [
                     0, 0,
                             0, 0,
                                      0, 0,
                                                      0; ...
       1,
\nabla 1
     -1/R1, (1/R2 + 1/R1), -1, 0, 0,
                                       0, 0,
                                                       0; ...
V2
                     1, 0, -1, 0,
        0,
                                       0, 0,
                                                       0; ...
I1
        0,
                     0, -1, 1/R3, 0,
                                                       0; ...
                                       0, -1,
V3
        0,
                    0, 0, 0, -a,
                                       1, 0,
                                                       0; ...
I3
                    0, 0, 1/R3, -1,
                                       0, -1,
        0,
                                                       0; ...
V4
                     0, 0,
                             0, 0,
                                       0, 1,
        0,
                                                       0; ...
In
        0,
                     0, 0,
                             0, 0, -1/R4, 0, (1/R4 + 1/R0)];
 %Vo
% Gaussian Pulse Function
mag = 1;
dev = 0.03;
delay = 0.06;
Flist = zeros(8,1,timecuts);
for count = 1:1:timecuts
   Flist(1,1,count) = mag*exp(-((count*dt-delay)/dev)^2); for
gaussian pulse
   Flist(7,1,count) = 0.001*randn;
end
Vlist = zeros(8,1,timecuts);
for count = 2:1:timecuts
   A = C/dt +G;
   Vlist(:,:,count) = A(C*Vlist(:,:,count-1)/dt +Flist(:,:,count));
end
V1list(1,:) = Vlist(1,1,:);
V2list(1,:) = Vlist(2,1,:);
ILlist(1,:) = Vlist(3,1,:);
I3list(1,:) = Vlist(4,1,:);
V4list(1,:) = Vlist(5,1,:);
Inlist(1,:) = Vlist(7,1,:);
Volist(1,:) = Vlist(8,1,:);
figure(17)
plot((1:timecuts).*dt,Volist(1,:))
```


```
ylabel('Voltage')
title('Vout of Gaussian Pulse with In and Cn timesteps=10000')
plot((1:timecuts).*dt,V1list(1,:))
hold off
figure(18)
g = abs(fftshift(fft(Volist(1,:))));
plot(((1:length(g))/timecuts)-0.5,g)
xlim([-0.005 0.005])
xlabel('Frequency')
ylabel('Magnitude')
title('Q3: Fourier Transform of Output')
disp('Q3: Increasing the value of Cn reduces the overall output of the
 circuit.')
Question 3: G and C matrices:
  Columns 1 through 7
    1.0000
                    0
                               0
                                         0
                                                    0
                                                               0
                                                                         0
   -1.0000
              1.5000
                        -1.0000
                                         0
                                                    0
                                                               0
                                                                          0
               1.0000
         0
                                   -1.0000
                                                    0
                                                               0
                                                                          0
                               0
                        -1.0000
                                    0.1000
         0
                    0
                                                    0
                                                               0
                                                                   -1.0000
         0
                    0
                               0
                                         0 -100.0000
                                                         1.0000
                                                                         0
         0
                    0
                               0
                                    0.1000
                                             -1.0000
                                                               0
                                                                   -1.0000
         0
                    0
                                                                    1.0000
                               0
                                         0
                                                    0
                                                               0
         0
                    0
                               0
                                         0
                                                    0
                                                       -10.0000
                                                                         0
  Column 8
         0
         0
         0
         0
         0
         0
         0
   10.0010
  Columns 1 through 7
         0
                               0
                    0
                                         0
                                                    0
                                                               0
                                                                         0
   -0.2500
               0.2500
                               0
                                                    0
                                         0
                                                               0
                                                                          0
                        -0.2000
         0
                    0
                                         0
                                                    0
                                                               0
                                                                          0
         0
                    0
                               0
                                    0.0000
                                                    0
                                                               0
                                                                          0
         0
                    0
                               0
                                         0
                                                    0
                                                               0
                                                                         0
         0
                    0
                               0
                                    0.0000
                                                    0
                                                               0
                                                                          0
                    0
                                                    0
                                                                          0
         0
                               0
                                         0
                                                               0
         0
                               0
                                         0
  Column 8
```


xlabel('Time(secs)')

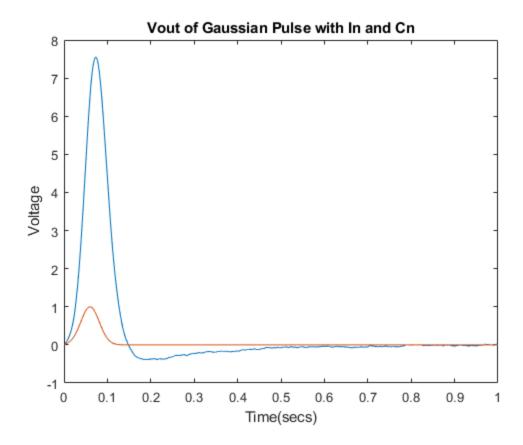
 ${\it Q3:}$ Increasing the value of Cn reduces the overall output of the circuit.




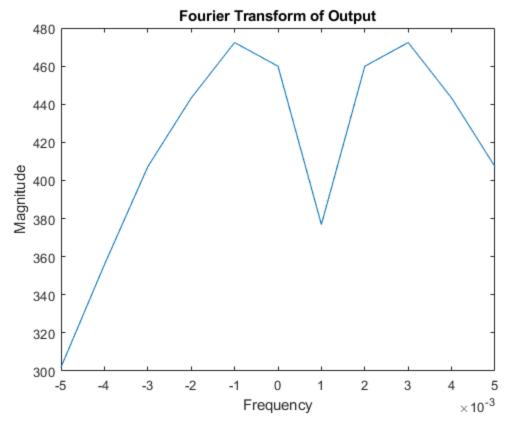


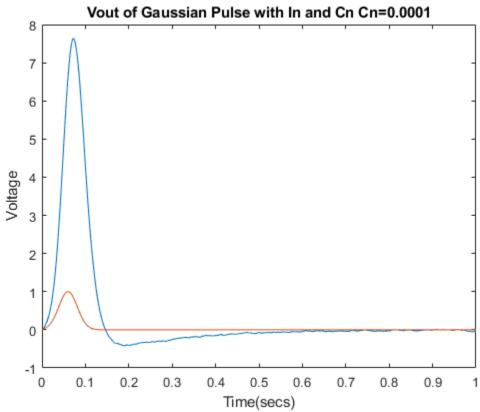


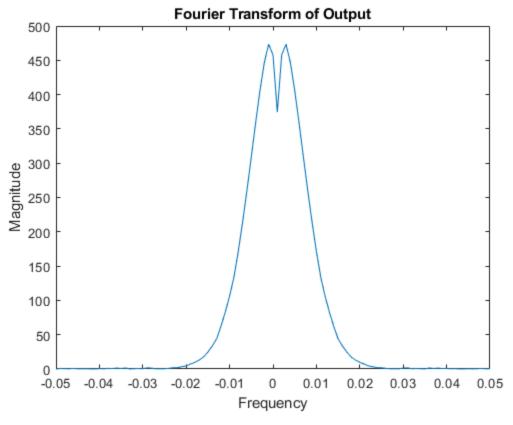


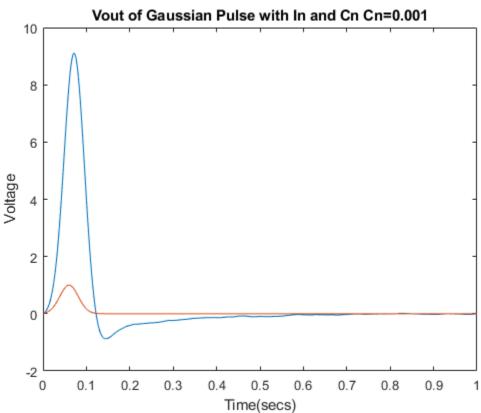


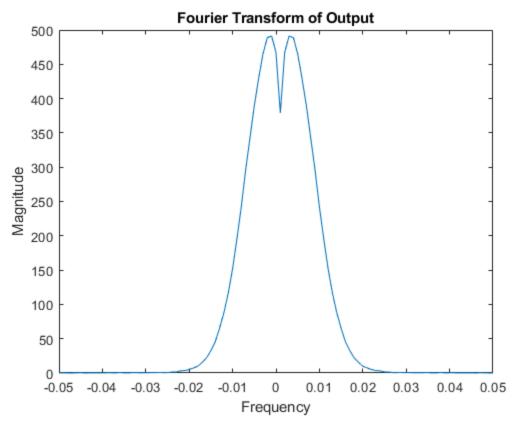


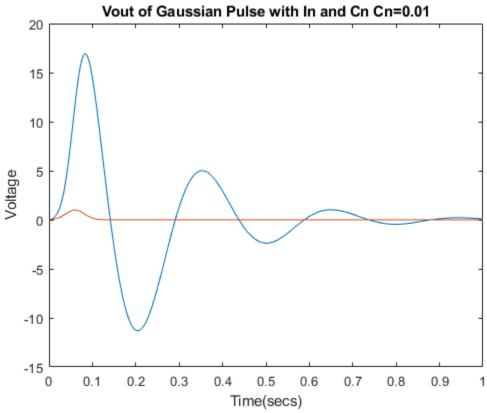


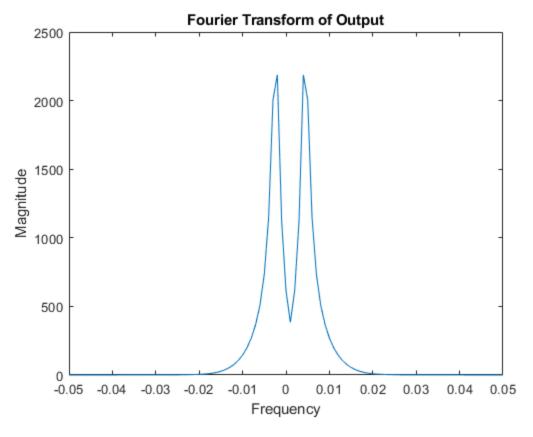

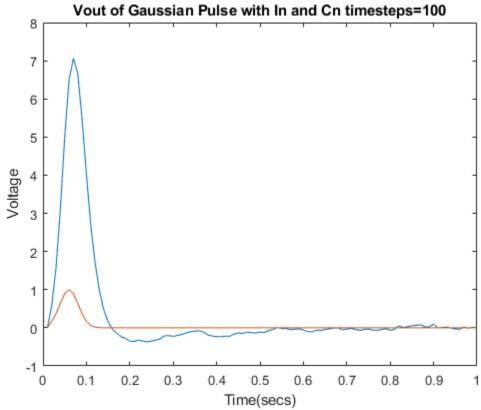

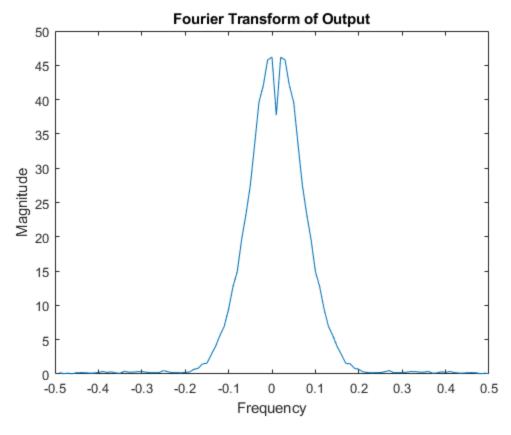

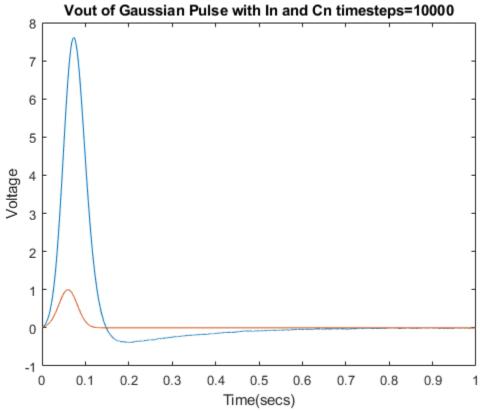

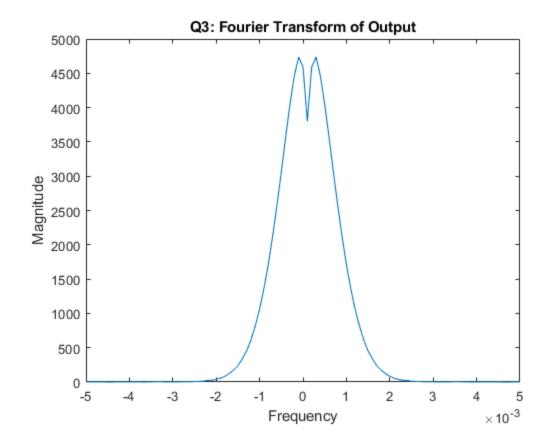

Published with MATLAB® R2018a